

## TD 2 : Construction of a real computer

---

### 1 Introduction

Continuing from last week's Exercise 3, in this lab, we will try to build a small computer starting from a NAND gate. To do this we will build increasingly complicated logical units until we have a computer capable of running programs. For this lab, we will use a Hardware Simulator. Its role will be to check that your logical units (*chips*) are well implemented. In addition, it will also help you with your debugging your chips.

The language in which you will write your chips is a DSL (Domain Specific Language), i.e. a language specifically dedicated to the writing of your chips. In the next section, this language will be briefly introduced so that you can start writing your first chips.

Each chip consists of three files :

- `XXX.hd1` : this is the file that you will write the code of your chips in.
- `XXX.tst` : this is a pre-written file which contains tests to verify if your code is right.
- `XXX.cmp` : this is also pre-written with the output of the test file.

The last two files are used by the Hardware Simulator to check the correctness of your chips. So for the most part, you will only edit files with the extension `.hd1`.

### Using the Hardware Simulator

Once the Hardware Simulator is started, to check your chip you have to follow these steps :

- Click on the **load chip** button to load the `.hd1` file
- Click on the **load script** button to load the `.tst` file
- Finally, click the **run** button (blue double-arrow) to run the tests

To save time, you can select the **no animation** button in the **animation** menu.

### Plan

This TP is divided into 4 sections :

1. In Section 3, you have to implement the basic chipset : And, Or, ...
2. In Section 4, we are interested in the conception of an ALU (Arithmetic Logic Unit)
3. In Section 5, we are interested in non-sequential chips in order to create the memory (RAM) of our computer
4. In section 6, we will bring together the different CHIPS written in the previous sections to build the computer.

You can find the zip folder containing all the requisite files here : <https://www.amritasuresh.github.io/teaching/bootstrap.tar.gz>.

## 2 Hardware Language

*Hardware Language* is a language that allows you to program chips. All the chips you are going to write respect the following format (example of the AND gate) :

```
/**
 * And gate:
 * out = 1 if (a == 1 and b == 1)
 *      0 otherwise
 */

CHIP And {
    IN a, b;
    OUT out;

    PARTS:
    //TODO
}
```

Each chip begins with a comment summarizing the expected behavior of the chip. Then, the code of a chip is divided into three parts :

- *IN* : this line gives names to the input pins. Here, the AND gate has two input pins named a and b
- *OUT* : this line gives names to the output pins. Here, the AND gate has a single output pin named out
- *PART* : This part contains the program you are going to write to implement the chips. This part is made up of a sequence of `texttt` instructions (described below) separated by semicolons.

The format of an instruction is as follows :

```
XXX(ipin1=var1, ipin2=var2, ..., opin1=var3, opin2=var4, ...)
```

The semantics of this instruction is that it calls the chip `XXX` :

- it connects to the input pin `ipin1` the pin `var1`, to the input pin `ipin2` the pin `var2`.
- `var3` is the new name of the output pin `opin1`, and `var4` is the new name of the output pin `opin2`

For the first two sections, it is expected that `var3` and `var4` are new names (new variables are created), while `var1` and `var2` are names that must already exist.

For example, when you want to create a new chip and you want to use the AND chip, you can write the following instruction :

```
...
AND(a=a1,b=a2, out=outand)
```

assuming that the variables `a1` and `a2` already exist.

## 3 Basic chips

We suppose in this section that the NAND chip is already constructed. Its interface is as follows :

```
/**
 * Nand gate:
 * out = 1 if (a == 0 and b == 0)
 *      0 otherwise
 */

CHIP Nand {
    IN a, b;
```

```

OUT out;

PARTS:
BUILTIN
}

```

This is the only chip that you can use at the start. Once you have correctly implemented a chip, it can be used to implement later chips. The comments at the start of each chip are self-explanatory, so there are no additional comments required for the construction. However, the below order is a suggested order to efficiently implement the necessary chips :

NOTE- The most efficient implementation (in terms of number of components used) is given in the brackets. As this will be part of your final project, the most efficient implementation will be awarded more points than a less optimal one.

1. Not (1 instruction)
2. And (2 instructions)
3. Or (3 instructions)
4. \*Or8Way (7 instructions)
5. Xor (5 instructions)
6. \*Not16 (16 instructions)
7. \*And16
8. \*Or16
9. Mux (4 instructions)
10. \*Mux16 (16 instructions)
11. Mux4Way16 (3 instructions)
12. \*Mux8Way16 (3 instructions)
13. DMux (3 instructions)
14. DMux4Way (3 instructions)
15. \*DMux8Way (5 instructions)

## 4 ALU

### Adder

From the basic bricks that we built in the previous section, we will try to build a logical arithmetic unit (ALU). Our arithmetic unit will be able to add two binary integers coded on 16 bits, but not only. It could increment / decrement, do bitwise operations like  $x \ \& \ y$  or  $x \ | \ y$ . For this, a first objective will be to recode a 16-bit adder. For this, you will have to implement the following chips :

1. HalfAdder (2 instructions)
2. FullAdder (3 instructions)
3. Add16 (16 instructions)
4. \* Inc16 (1 instruction)

### ALU

Once these gates have been implemented, we are interested in the ALU. The idea of this chip is to take two vectors encoded on 16 bits as inputs  $x$  and  $y$  and to calculate at output a vector of 16 bits  $out(x, y)$ .  $out$  is a function which is parameterized by 6 flags (as shown in Fig. 4).

```

Chip name: ALU
Inputs:    x[16], y[16],      // Two 16-bit data inputs
              zx,                // Zero the x input
              nx,                // Negate the x input
              zy,                // Zero the y input
              ny,                // Negate the y input
              f,                // Function code: 1 for Add, 0 for And
              no                 // Negate the out output
Outputs:  out[16],           // 16-bit output
              zr,                // True iff out=0
              ng                 // True iff out<0

```

FIGURE 1 – The Arithmetic Logic Unit

**Preliminaires :** A few questions before embarking on the implementation (the order of the flags is the one presented above) :

- What is the function  $out(x, y)$  when we pass the flags as a vector  $(0, 1, 0, 1, 0, 1)$  ?
- What is the function  $out(x, y)$  when we pass the flags as a vector  $(0, 0, 1, 1, 0, 1)$  ?
- What is the function  $out(x, y)$  when we pass the flags as a vector  $(1, 1, 1, 1, 1, 1)$  ?
- Is it possible to calculate  $x + 1$  ?
- Is it possible to calculate  $x - 1$  ?
- Is it possible to calculate  $x - y$  ?

**Implementation :** Now, implement the following chip :

1. ALU (13 instructions)

## 5 Memory

This part is interested in logic gates whose behavior depends on time. In other words, one of the output pins can be connected to one of the input pins. This implies that in practice, this style of chip uses a clock, which will regulate the electrical signal. However, in our case, and to simplify the design of our chips, we are not going to manipulate the clock directly. Instead, we'll assume that we have a *built-in* chip, like the `nand` gate given to us. This chip, called DFF copies its input to its output at each clock *tick* (see Fig. 5). Note that using a clock is the same as discretizing time.



$$out(t) = in(t-1)$$

FIGURE 2 – DFF

For this section, program the chips in the following order :

1. Bit (2 instructions)
2. Register (16 instructions)

```

Chip Name:
Keyboard    // Memory map of the physical keyboard.
            // Outputs the code of the currently
            // pressed key.

Output:
out[16]     // The ASCII code of the pressed key, or
            // one of the special codes

Function:
Outputs the code of the key presently pressed on the
physical keyboard.
Comment:
This chip is continuously being refreshed from a
physical keyboard unit (simulators must simulate this
service).

```

FIGURE 3 – Keyboard

3. PC (5 instructions)
4. RAM8 (10 instructions)
5. RAM64 (10 instructions)
6. RAM512 (10 instructions)
7. RAM4K (10 instructions)
8. RAM16K (6 instructions)

## 6 Computer

In this part, we will reuse the RAM built in the previous part as well as our ALU to build a *real* computer. Our computer will use two external peripherals : a keyboard and a screen whose specification is given to you respectively in Fig. 3 and Fig. 4. Note that the Hardware Simulator manages the inputs /outputs for you. In our case, we will not take care of the entries. In the Hardware Simulator, under the option **View** you can select **Screen** to see what some tests produce (like `ComputerRect-external.tst`). In addition, in our architecture, we must load our program in memory which will be different from the RAM. Here it will be the ROM. For that, we will also use a *built-in* chip which will simulate this component see Fig. 5. Implement the chips in the following order :

1. Memory (7 instructions)
2. CPU (20 instructions)
3. Computer (3 instructions)

Afin de vous aider, vous trouverez en Fig. 6, un schéma qui résume le comportement interne du CPU.

```

Chip Name:
Screen      // Memory map of the physical screen
Inputs:
in[16],     // What to write
load,       // Write-enable bit
address[13] // Where to write
Output:
out[16]     // Screen value at the given address
Function:
Functions exactly like a 16-bit 8K RAM:
1. out(t)=Screen[address(t)](t)
2. If load(t-1) then Screen[address(t-1)](t)=in(t-1)
(t is the current time unit, or cycle)
Comment:
Has the side effect of continuously refreshing a 256
by 512 black-and-white screen (simulators must
simulate this device). Each row in the physical
screen is represented by 32 consecutive 16-bit words,
starting at the top left corner of the screen. Thus
the pixel at row r from the top and column c from the
left (0<=r<=255, 0<=c<=511) reflects the c%16 bit
(counting from LSB to MSB) of the word found at
Screen[r*32+c/16].

```

FIGURE 4 – Screen

```

Chip Name:
ROM32K      // 16-bit read-only 32K memory
Input:
address[15] // Address in the ROM
Output:
out[16]     // Value of ROM[address]
Function:
out=ROM[address] // 16-bit assignment
Comment:
The ROM is preloaded with a machine language program.
Hardware implementations can treat the ROM as a
built-in chip. Software simulators must supply a
mechanism for loading a program into the ROM.

```

FIGURE 5 – ROM

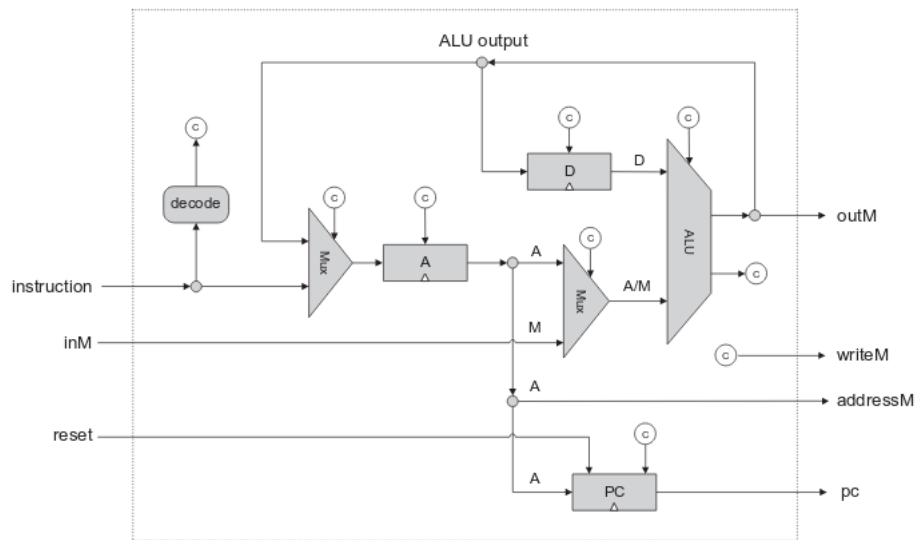


FIGURE 6 – CPU